

Exercice n°1 :

$$1) W_q = P_a \times t \Rightarrow P_a = \frac{W_q}{t} = \frac{39600}{360} = 110 \text{ kW}$$

$$W_r = Q_a \times t \Rightarrow Q_a = \frac{W_r}{t} = \frac{32666,4}{360} = 90,74 \text{ kVAR}$$

$$\tan(\varphi) = \frac{Q_a}{P_a} = \frac{90,74}{110} = 0,825.$$

$$\varphi = 39,5^\circ \Rightarrow \cos(\varphi) = 0,77.$$

$$\left| \begin{array}{l} P_a = 3V I \cos(\varphi) = \sqrt{3} V I \cos(4) \\ I = \frac{P_a}{\sqrt{3} \cdot V \cdot \cos(4)} = \frac{110 \times 10^3}{\sqrt{3} \cdot 400 \times 0,77} = 206 \text{ A} \end{array} \right.$$

$$2) \cos(\varphi') = 0,707 = \frac{\sqrt{2}}{2}$$

$$P_t = \sqrt{3} \cdot U' \cdot I \cdot \cos(\varphi') = \sqrt{3} \cdot 470 \cdot 206 \cdot 0,707 = 118,6 \text{ kW}$$

$$W_t = \frac{P_t}{\sqrt{3} \cdot I \cdot \cos(\varphi')} = 118,6 \text{ kVAR}$$

$$P_t = P_a + 3R I^2 \Leftrightarrow R = \frac{P_t - P_a}{3 \cdot I^2} = \frac{8,6 \times 10^3}{3 \times 206^2} = 67,5 \Omega$$

$$Q_t = Q_a + 3 \cdot L_w \cdot I^2 \Leftrightarrow L_w = \frac{Q_t - Q_a}{3 \cdot I^2} = \frac{(118,6 - 90,74) \times 10^3}{3 \times 206^2} = 0,22 \Omega.$$

$$3) \text{Pertes en ligne : } P_t - P_a = 8,6 \text{ kW}$$

$$\text{Pertes : } \frac{8,6}{118,6} = 0,0725 \text{ soit } 7,25 \%$$

$$u) \quad P_a = P_a' \quad Q_a' = Q_a + Q_a = P_a' \tan(\varphi') = P_a \tan(\varphi)$$

$$Q_a = P_a \tan(\varphi)$$

$$Q_c = Q_a' - Q_a = P_a (\tan(\varphi') - \tan(\varphi))$$

$$\cos(\varphi') = 0,9 \Rightarrow \tan(\varphi') = 0,484 \Rightarrow \varphi' = 25,8^\circ$$

$$\tan(\varphi) = 0,825$$

$$Q_c = 110 (0,484 - 0,825) = [-37,5 \text{ kVAR}] \quad \begin{array}{l} \text{Energie reactive fournie} \\ \text{par les condensateurs} \end{array}$$

Pour 1 condensateur,



$$\sqrt{\frac{I}{C_w}} = \frac{V}{1/C_w} = V_{CW} \quad \text{= 1}$$

$$Q = V I \cdot \sin(\varphi) = V \cdot V C_w = V^2 C_w$$

$$Q_c = 3 \cdot V^2 C_w$$

$$Q = \frac{Q_c}{3V^2 C_w} = \frac{37590}{3 \times 230^2 \times 2\pi \cdot 50} \Leftrightarrow C_c = 752,15 \mu F$$

En étoile.

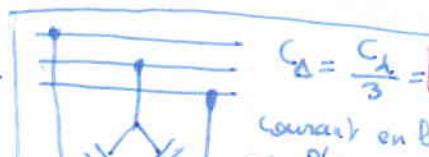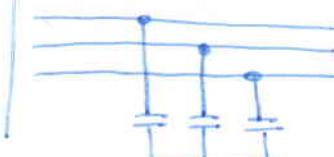

$$C_d = \frac{C_c}{3} = 250,7 \mu F$$

en triangle

$$I' = \frac{P_a'}{\sqrt{3} \cdot V \cdot \cos(\varphi')} = \frac{110 \cdot 10^3}{\sqrt{3} \cdot 400 \cdot 0,9} = 176 \text{ VA}$$


$$5) \text{ Powers: } 3 \cdot R \cdot I^2 = 3 \times 0,0675 \times 186^2 = 6,3 \text{ kW}$$

$$P_t' = P_a' + \text{Power} = 110 + 6,3 = 116,3 \text{ kW}$$

$$\text{Power} = \frac{6,3}{116,3} = 0,053 = 5,3\%$$

$$6) \text{ Volume: } 125 \times 250 \times 662 = 14,437,500 \text{ mm}^3 = 0,014 \text{ m}^3$$

Exercise n° 2:

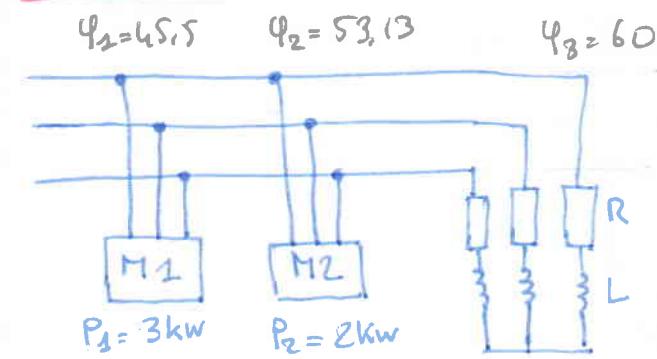


$$3) \underline{V}_{12} = \underline{V}_1 - \underline{V}_2 = V(1 - e^{j240^\circ})$$

$$\underline{V}_{12} = V\left(1 + \frac{1}{2} + \frac{\sqrt{3}}{2}j\right) = V\sqrt{3}e^{j\frac{\pi}{6}}$$

$$\underline{V}_{23} = \underline{V}_2 - \underline{V}_3 = V(e^{j240^\circ} - e^{j120^\circ}) = V\sqrt{3}e^{-j\frac{\pi}{2}}$$

$$\underline{V}_{31} = \underline{V}_3 - \underline{V}_1 = V(e^{j120^\circ} - 1) = V\sqrt{3}e^{j\frac{5\pi}{6}}$$

4) Schema monophasé équivalent.

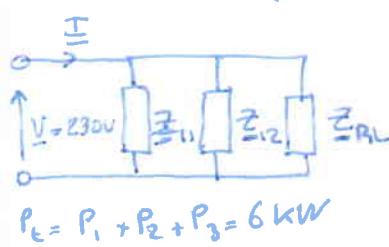

$$6) \cos(\phi_T) = \frac{P_t}{S_t} = \frac{6}{9,57} = 0,63$$

$$\phi_T = 51,2^\circ$$

$$9) \begin{cases} P_T = P_{AC}^1 + P_{BC}^2 \\ Q_T = \sqrt{3}(P_{AC}^1 - P_{BC}^2) \end{cases} \Leftrightarrow \begin{cases} P_T = P_{AC}' + P_{BC}^2 \\ \frac{Q_T}{\sqrt{3}} = P_{AC}' - P_{BC}^2 \end{cases}$$

$$11) Q_C = P_T (\tan(\phi_T) - \tan(\phi)) = 6 (0,6 - 0,24) -$$

$$Q_C = -5,04 \text{ kVAR}$$

$$C = \frac{Q_C}{3U^2w} = \frac{5040}{3 \times 400^2 \times 2\pi \times 50} = 33,7 \text{ mF.}$$

$$1) \underline{v}_1(t) = \hat{V} \cos(\omega t) = V\sqrt{2} \cdot \cos(\omega t)$$

$$\underline{v}_2(t) = V\sqrt{2} \cos(\omega t - \frac{2\pi}{3})$$


$$\underline{v}_3(t) = V\sqrt{2} \cos(\omega t - \frac{4\pi}{3})$$

$$\underline{V}_1 = V$$

$$\underline{V}_2 = V e^{j240^\circ}$$

$$\underline{V}_3 = V e^{j120^\circ}$$

2) 8)

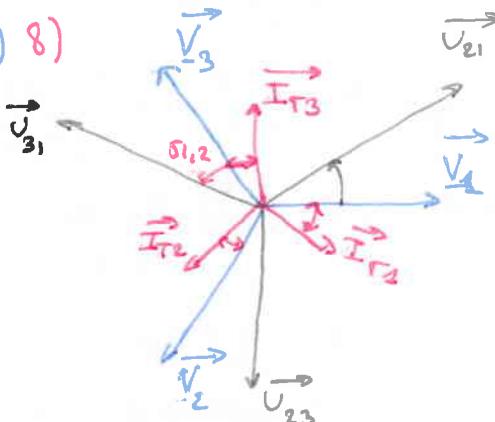

5)

$$P_t = P_1 + P_2 + P_3 = 6 \text{ kW}$$

$$Q_t = P_1 \tan(\phi_1) + P_2 \tan(\phi_2) + P_3 \tan(\phi_3)$$

$$Q_t = 3 \times 1,02 + 2 \times 1,33 + 1 \times 1,73 = 74,59,3 \text{ VAR.}$$

$$S_t = \sqrt{P_t^2 + Q_t^2} = 95,72,9 \text{ VA.}$$

$$7) I_t = \frac{S_t}{3V} = \frac{95,72,9}{3 \times 230} = 13,9 \text{ A} \Leftrightarrow I_t = 13,9 e^{-j51,2^\circ}$$

$$P_{AC}^1 = \frac{1}{2} \left(P_t + \frac{Q_t}{\sqrt{3}} \right) = 51,53 \text{ W}$$

$$P_{BC}^2 = P_t - P_{AC}^1 = 86,8 \text{ W.}$$

$$12) P_t' = P_t = 6 \text{ kW} \Rightarrow I_t' = \frac{P_t'}{\sqrt{3} \cdot U \cdot \cos(\phi)}$$

$$Q_t' = Q_t + Q_C \Rightarrow$$

$$I_t' = \frac{6 \times 10^3}{\sqrt{3} \cdot 400 \times 0,93} = 9,35 \text{ A}$$

$$I_t' = 9,35 e^{-j21,5^\circ}$$