

Exos n°1:

$$1) P_T = P_{13} + P_{23} = 15 \text{ kW} + 5 \text{ kW} = 20 \text{ kW}$$

$$Q_T = \sqrt{3} |P_T| = \sqrt{3} 20 \cdot 10^3 = 17,32 \text{ kVAR.}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \sqrt{20^2 + 17,32^2} = 26,46 \text{ kVA.}$$

$$2) \cos(\varphi_T) = \frac{P_T}{S_T} = 0,76 \Leftrightarrow \varphi_T = 40,9^\circ \Leftrightarrow \tan(\varphi_T) = 0,87.$$

$$3) \underline{I}_T = \frac{S_T}{3V} = 38,34 \text{ A.}$$

$$\underline{I}_1 = \underline{I}_T e^{-j\varphi_T} = 38,34 e^{-j40,9^\circ} \text{ A.}; \underline{I}_2 = a^2 \underline{I}_1; \underline{I}_3 = a \underline{I}_1$$

$$4) \cos(\varphi_g) = 0,93 \quad C_\Delta = ?$$

$$P_G = P_T.$$

$$Q_C = 3C_\Delta \omega U^2 \Leftrightarrow C_\Delta = \frac{Q_C}{3\omega U^2}$$

$$Q_G < Q_T = Q_T - Q_C$$

$$S_G$$


$$Q_C = Q_T - Q_T' = P_T \tan(\varphi_T) - P_T \tan(\varphi_g) = 20 \cdot 10^3 \cdot 0,87 - 20 \cdot 10^3 \cdot 0,4 = 9416 \text{ VAR.}$$

$$C_\Delta = \frac{Q_C}{3\omega U^2} = 64,64 \text{ pF.}$$

$$\underline{I}'_1 = \underline{I}'_T e^{-j\varphi'_T}; \underline{I}'_2 = a^2 \underline{I}'_1; \underline{I}'_3 = a \underline{I}'_1$$

$$5) P_T' = P_T = 3V \underline{I}'_T \cos(\varphi'_T)$$

$$\underline{I}'_T = \frac{P_T}{\cos(\varphi'_T) 3V} = 31,17 \text{ A} < \underline{I}_T = 38,34 \text{ A.} \quad |\underline{I}'_1| = |\underline{I}'_T| = e^{-j\varphi'_T} = 31,17 e^{-j21,6^\circ} \text{ A.}$$

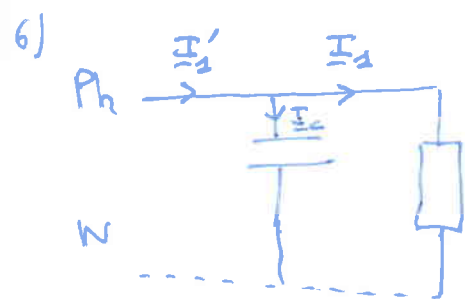

$$7) \underline{Z}_T = ? \quad C_y = ? \quad \underline{Z}_T = z_T e^{j\varphi_T}$$

$$C_y \quad \underline{Z}_T = \frac{V_i}{\underline{I}_1} = \frac{V}{\underline{I}_T e^{-j\varphi_T}} = \frac{V}{\underline{I}_T} e^{j\varphi_T}$$

$$Q_C = 3C_\Delta \omega U^2 = 3C_y \omega V^2$$

$$\text{où } U = V\sqrt{3}$$

$$3C_\Delta \omega (3V)^2 = 3C_y \omega V^2$$

$$\underline{Z}_T = \frac{V}{\underline{I}_T} = \frac{230}{38,34} = 6 \Omega.$$

$$\underline{Z}_T = 6 e^{j40,9^\circ}$$

$$C_y = 3C_\Delta$$

$$C_y = 193 \text{ pF}$$



$$\underline{Z} = z_T e^{j\varphi_T} = \underbrace{R + jL\omega}_{z_T \cos(\varphi_T)} + j \underbrace{L\omega}_{z_T \sin(\varphi_T)}$$

$$P_T = 3R I_T^2 = 20 \text{ kW}$$

$$Q_T = 3L\omega I_T^2 = 17,32 \text{ kVAR}$$

$$R = z_T \cos(\varphi_T) = 4,53 \Omega$$
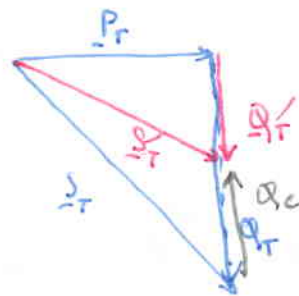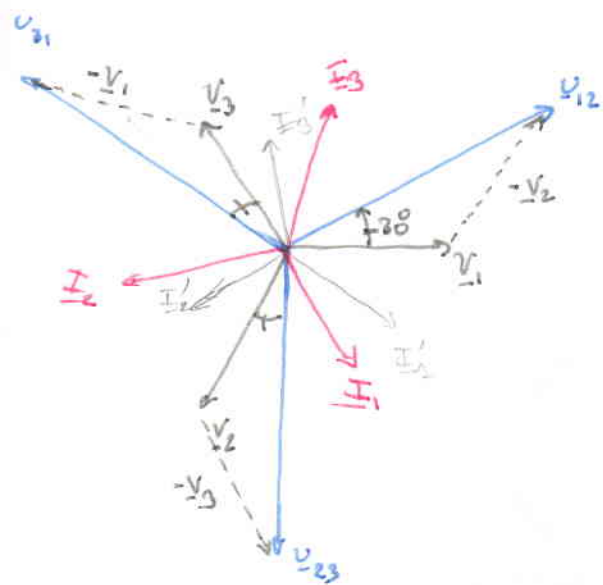
$$L\omega = z_T \sin(\varphi_T) = 3,93 \Omega$$



Exos n°2:

$\sqrt{3} \rightarrow$ déphasage 30°

$$U_{12} = U_e e^{j30^\circ}; U_{23} = a^2 U_{12}; U_{31} = a U_{12} \quad | \quad \underline{I}_1 = \underline{I}_T e^{-j\varphi_T}; \underline{I}_2 = a^2 \underline{I}_1; \underline{I}_3 = a \underline{I}_1$$

1) $P_T = P_{10}^2 + P_{23}^2 = 736 \text{ W}$

$$Q_T = \sqrt{3} (P_{13}^2 - P_{23}^2) = 1732 \text{ W}$$

2) $S_T = 3V I_T = \sqrt{P_T^2 + Q_T^2} = 1881, \text{ VA}$

$$\cos(\varphi_T) = \frac{P_T}{S_T} = 0,76 \rightarrow \varphi_T = 67^\circ$$

$$I_T = \frac{S_T}{3V} = 2,73 \text{ A} \quad \underline{I}_1 = I_T e^{-j\varphi_T} = 2,73 e^{-j67^\circ} \text{ A}$$

3) $I_T = I_T \sqrt{3} \Rightarrow I_T = \frac{I_T}{\sqrt{3}} = 1,57 \text{ A}$

4) $\underline{Z} = z e^{j\varphi_T} \rightarrow z = \frac{U}{I_T} = \frac{400}{1,57} = 254 \Omega$

$$\underline{Z} = \underbrace{z \cos(\varphi_T)}_R + j \underbrace{z \sin(\varphi_T)}_{L\omega} \quad \left\{ \begin{array}{l} R = 99,36 \Omega \\ L\omega = 233,79 \Omega \end{array} \right.$$

5) étoile $\Rightarrow V \parallel$ triangle $\Rightarrow U$

$$\underline{I}'_1 = \underline{I}'_T e^{-j\varphi_T} \quad I'_T = \frac{V}{z} = \frac{230}{254} = 0,91 \text{ A}$$

6) $P'_T = 3V I'_T \cos(\varphi_T) = 3R I'^2_T = 244,3 \text{ W}$
 $Q'_T = 3V I'_T \sin(\varphi_T) = 3L\omega I'^2_T = 575 \text{ VAR}$
 $\Rightarrow \left\{ \begin{array}{l} P_T = 3P'_T \\ Q_T = 3Q'_T \end{array} \right.$