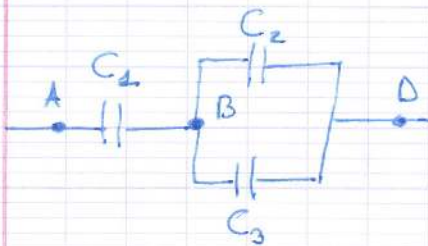


Regime variable:

II - Condensateur:

$$E_{elec} = \frac{1}{2} C u \quad \begin{cases} E_{elec}: J \\ C: Farad \\ u: V \end{cases}$$

Association en parallele / serie




Entre les points B et D (associat° parallele):

$$C_{BD} = C_2 + C_3$$

Entre les points A et D (associat° serie):
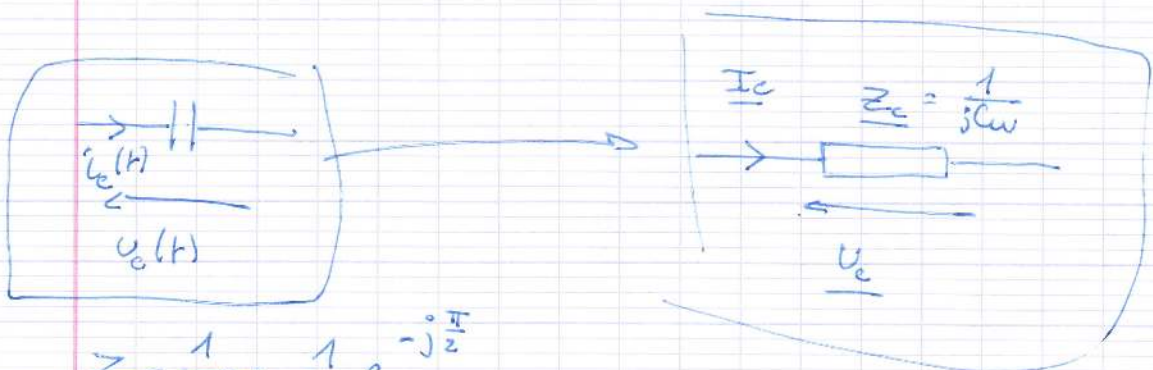
$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_{BD}} = \frac{C_2 + C_3}{C_1(C_2 + C_3)} \text{ soit } \frac{C_2(C_2 + C_3)}{C_1 + C_2 + C_3}$$



$$\underline{Z}_c = \frac{1}{j\omega C} = \frac{1}{\omega C} e^{-j\frac{\pi}{2}}$$


II 1 - Bobine:

$$u = L \frac{di}{dt} \quad \begin{cases} u = V \\ L = \text{Henri} \\ i = A \end{cases}$$


$$i(t) = \frac{U}{L} t$$

$$E_{\text{mag}} = \frac{1}{2} L i^2 \quad \begin{cases} E_{\text{mag}} = J \\ L = \text{Henri} \\ i = A \end{cases}$$

Association de bobine:

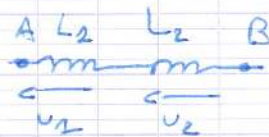

$$L = L_1 + L_2$$

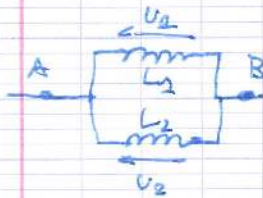


$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$$

II 1 - Associations de dipôles linéaires



$$u_2 = L \frac{di}{dt} + ri$$
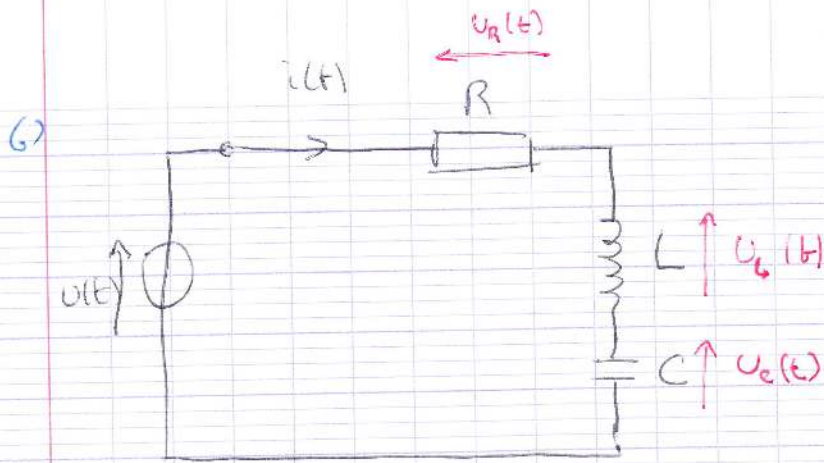
$$u = u_1 + u_2 = L \frac{di}{dt} + ri + u_2$$



$u_R(t) = R \cdot i(t) \Rightarrow$ la loi d'Ohm est applicable en instantané (vraisemblable)

$$u_L(t) = L \cdot \frac{di(t)}{dt}$$

$$i(t) = C \cdot \frac{dq(t)}{dt} \quad u_C(t) = \frac{q(t)}{C}$$

$$i(t) = \frac{dq(t)}{dt}$$

$$u(t) = R \cdot i(t) + L \frac{di(t)}{dt} + u_C(t)$$

$$u(t) = R \cdot \frac{dq(t)}{dt} + L \frac{d^2 q(t)}{dt^2} + \frac{1}{C} \cdot q(t)$$

$$u(t) = L \cdot \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q(t)$$

Equatⁿ homogène $L \cdot n^2 + Rn + \frac{1}{C} = 0$

$$\Delta = R^2 - \frac{4L}{C}$$

$\Delta > 0$

$$h_1 = \frac{-R + \sqrt{R^2 - \frac{4L}{C}}}{2L}$$

$$h_2 = \frac{-R - \sqrt{R^2 - \frac{4L}{C}}}{2L}$$

$\Delta < 0$

$$j_1 = \frac{-R + i\sqrt{\frac{4L}{C} - R^2}}{2L}$$

$$j_2 = \frac{-R - i\sqrt{\frac{4L}{C} - R^2}}{2L}$$

$\Delta = 0$


$$h_0 = \frac{-R}{2L}$$

$$u(t) = \frac{E}{\sqrt{1 + (R_2 C \omega)^2}} \sqrt{2} \sin(\omega t - \text{Arctan}(R_2 C \omega))$$

b)

$$u(t) = \frac{5V}{\sqrt{1 + (1,7332 \times 10^3 \times 10 \times 10^{-9} \omega)^2}} \sqrt{2} \sin(\omega t - \dots)$$


Exercice n°2

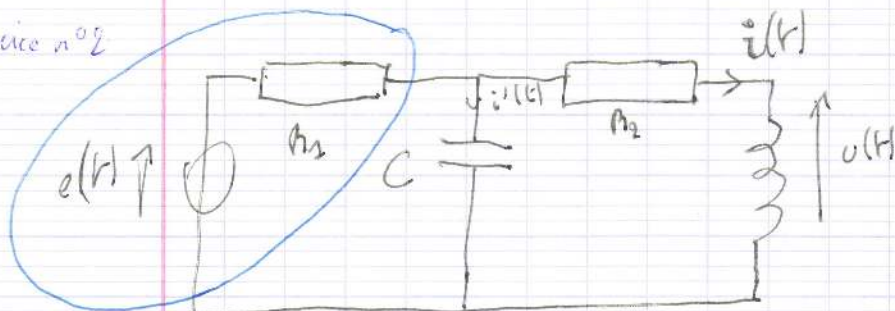

$$e(t) = E_m \sqrt{2} \sin(\omega t)$$

Equivalente

Thevenin - Norton

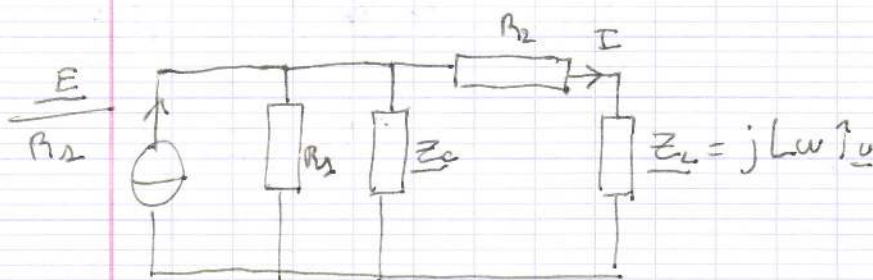

Pour déterminer de courant.


$$I = \frac{E}{R_1} \times \frac{1}{R_2 + jL\omega} \cdot \frac{1}{\frac{1}{R_2} + j\omega C + \frac{1}{R_2 + jL\omega}} = \frac{E}{R_2 + jL\omega} \cdot \frac{R_2 + jL\omega}{R_2(jL\omega C + R_2 + jL\omega) + 1}$$

$$= \frac{E}{R_2 + R_2 - R_2 L C \omega^2 + j(R_2 R_2 C \omega + L \omega)}$$

$$I = \frac{E}{\sqrt{(R_2 + R_2 - R_2 L C \omega^2)^2 + (R_2 R_2 C \omega + L \omega)^2}}$$

$$\varphi_I = \text{Arctan} \left(\frac{R_2 R_2 C \omega + L \omega}{R_2 + R_2 - R_2 L C \omega^2} \right)$$

Exercice n°3:

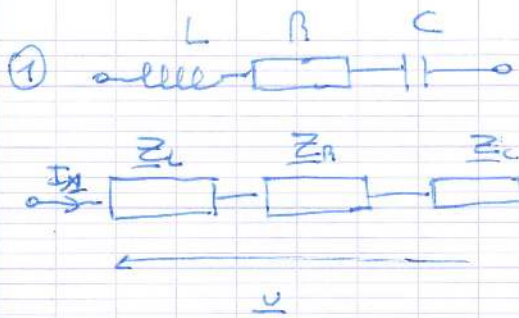

$$\begin{aligned} Z_1 &= Z_L + Z_R + Z_C \\ &= R + jL\omega - \frac{1}{C\omega} \end{aligned}$$

$$I_1 = \frac{U}{Z_1}$$


#Module

$$Z_2 = \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}$$


$$Z_2 = R + jL\omega$$



$$I_2 = \frac{U}{Z_2}$$

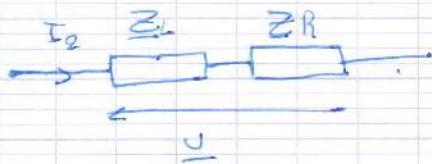

$$|Z_2| = Z_0 = \sqrt{R^2 + (L\omega)^2}$$

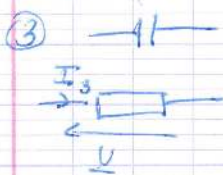

$$\begin{aligned} Z_3 &= j\left(-\frac{1}{C\omega}\right) = -\frac{j}{C\omega} \\ &= -j\left(\frac{1}{C\omega}\right) \\ I_3 &= \frac{U}{Z_3} \end{aligned}$$

$$Z_3 = \frac{1}{C\omega}$$

$$Z_1^2 = Z_2^2 = Z_3^2$$

$$R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2 = R^2 + (L\omega)^2 = \left(\frac{1}{C\omega}\right)^2$$

$$R^2 + (L\omega)^2 - \frac{2L}{C} + \left(\frac{1}{C\omega}\right)^2 = R^2 + (L\omega)^2 = \left(\frac{1}{C\omega}\right)^2$$

$$LC\omega^2 = \frac{1}{2}$$

$$(C\omega)^2 \cdot R^2 = (L\omega)^2 (C\omega)^2 = 1$$

$$(RC\omega)^2 = L^2 C^2 \omega^2 = 1$$


$$u_R(t) = R \cdot i(t)$$

$$u_L(t) = L \cdot \frac{di(t)}{dt}$$

$$u(t) = U \cdot \sqrt{2} \sin(\omega t) = U_m \sin(\omega t)$$

$$u(t) = R \cdot i(t) + L \frac{di(t)}{dt}$$

$$i(t) = I_m \sin(\omega t + \varphi)$$

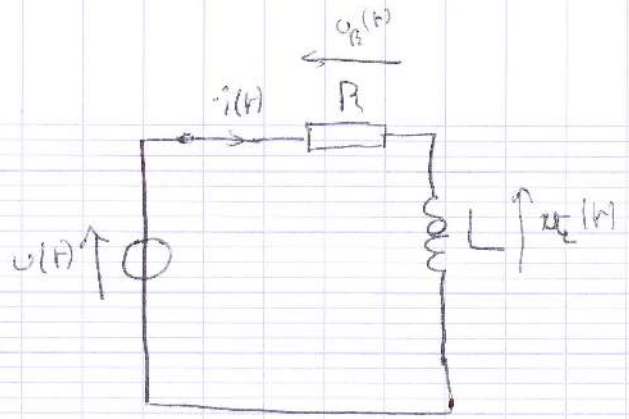

$$U_m \sin(\omega t) = R \cdot I_m \sin(\omega t + \varphi) + L \cdot \omega I_m \cos(\omega t + \varphi)$$

$$U_m \sin(\omega t) = I_m (R \sin(\omega t + \varphi) + L \omega \cos(\omega t + \varphi))$$

$$I_m = \frac{U_m \sin(\omega t)}{R \sin(\omega t + \varphi) + L \omega \cos(\omega t + \varphi)}$$

$$U_m \sin(\omega t) = R \cdot I_m \sin(\omega t) \cos(\varphi) - L \omega \cdot I_m \sin(\varphi) \sin(\omega t) + R \cdot I_m \sin(\varphi) \cos(\omega t) + L \omega I_m \cos(\varphi) \cdot \cos(\omega t)$$

$$U_m = R \cdot I_m \cos(\varphi) - L \omega I_m \sin(\varphi)$$

$$0 = R \cdot I_m \sin(\varphi) + L \omega \cdot I_m \cos(\varphi)$$

$$\tan \varphi = -\frac{L \omega}{R}$$

Z^e methode

$$\underline{U} = U e^{j\varphi} e^{j\omega t} = \underline{U}$$


$$\underline{U} = R \cdot \underline{I} + jL\omega \underline{I}$$

$$\underline{U} = (R + jL\omega) \cdot \underline{I}$$

$$\underline{I} = \frac{\underline{U}}{R + jL\omega} = \frac{U \cdot e^{j\omega t}}{\sqrt{R^2 + (L\omega)^2} e^{j \arctan(\frac{L\omega}{R})}}$$

$$U_R = R \cdot \underline{I}$$
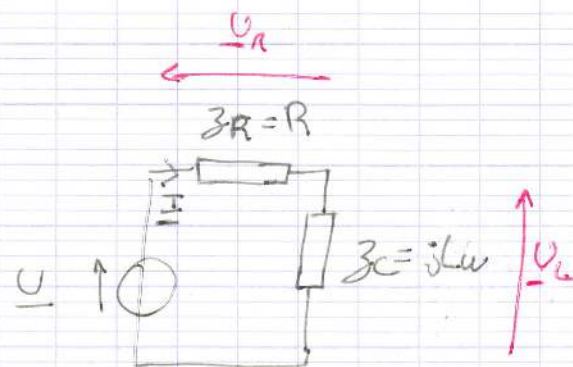
$$U_L = Z_L \cdot \underline{I} = jL\omega \times \underline{I}$$



$$I = \frac{U}{\sqrt{R^2 + (L\omega)^2}}$$


$$\varphi = -\text{Arctan}\left(\frac{L\omega}{R}\right)$$

$$\underline{I} = I \cdot e^{j\varphi} = \frac{U}{\sqrt{R^2 + (L\omega)^2}} e^{-j\text{Arctan}\left(\frac{L\omega}{R}\right)}$$


$$i(t) = I \sqrt{2} \cdot \sin(\omega t + \varphi) = \frac{U}{\sqrt{R^2 + (L\omega)^2}} \cdot \sqrt{2} \cdot \sin\left(\omega t - \text{Arctan}\left(\frac{L\omega}{R}\right)\right)$$

Le Filtrage

Exercice n° 1

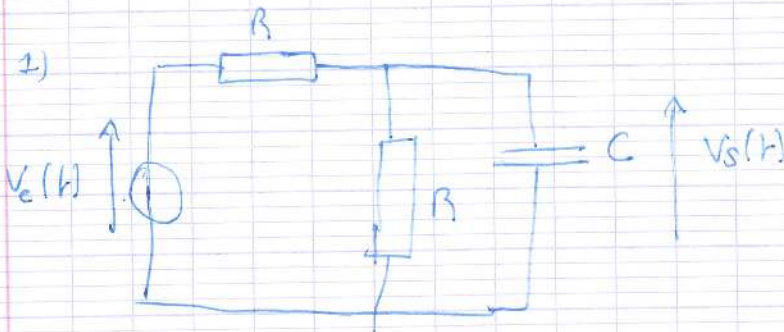

BF

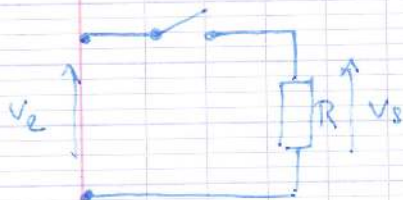

$$i_C = 0A$$

$$\text{donc } V_s = 0V$$

$$A(\omega \rightarrow 0) = \frac{0}{V_e} = 0$$


Filtre passe bas

HF






$$V_s = V_e$$
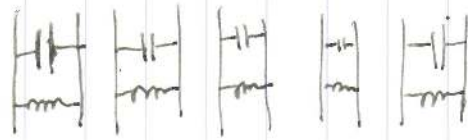
$$A(\omega \rightarrow \infty) = \frac{V_s}{V_e}$$



$$(RC\omega)^2 = \frac{3}{4} \Rightarrow RC\omega = \frac{\sqrt{3}}{2}$$

Exercice n°5 :

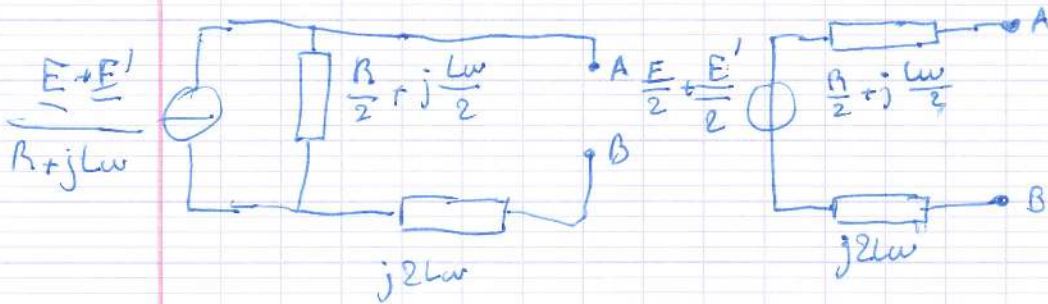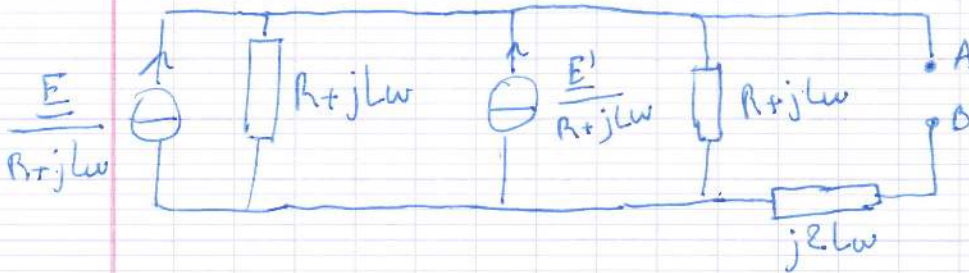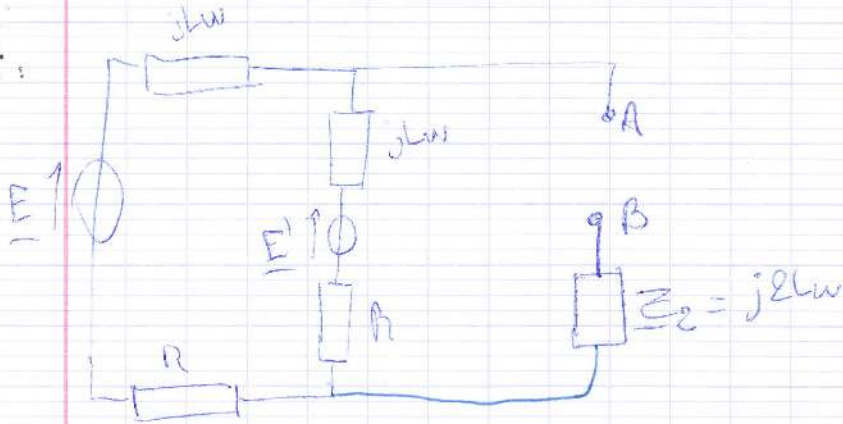

$$\underline{E} = \frac{E}{\sqrt{2}} \cdot e^{j0}$$

$$\underline{E}' = \frac{E}{\sqrt{2}} \cdot e^{-j\frac{\pi}{2}} = \frac{E}{\sqrt{2}} \cdot (-j)$$


forme riège

$$\underline{E} + \underline{E}' = \frac{E}{\sqrt{2}} (1-j)$$


$$e(t) = E \cdot \cos(\omega t)$$

$$e'(t) = E \cdot \sin(\omega t)$$
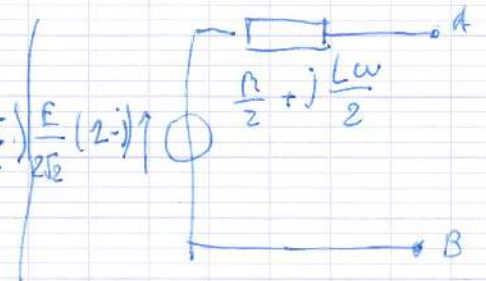
$$= E \cdot \cos(\omega t - \frac{\pi}{2})$$


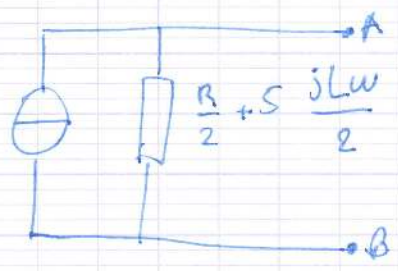
$$\frac{\frac{E}{2\sqrt{2}} \cdot (1-j)}{\frac{R}{2} + j\frac{L\omega}{2}}$$



$$\underline{V} = \frac{\frac{E_1}{Z_C} + \frac{E_2}{Z_A}}{\frac{1}{Z_C} + \frac{1}{Z_A} + \frac{1}{Z_A + Z_C}} = \frac{E_1 \cdot j\omega + \frac{E_2}{R_2}}{j\omega + \frac{1}{R_2} + \frac{1}{R_1 + j\omega}}$$

$$\frac{1}{Z_C} = j\omega$$