

Retroaction < 0 \Rightarrow Mode linéaire

$$V^+ = V^- = 0 \text{ ou } v_e$$

$$V^- = \frac{V_s}{\frac{1}{R_1} + \frac{1}{R_0}} = \frac{R_2 V_s}{R_1 + R_0} = v_e$$


$$A_{2v} = \frac{v_s}{v_e} = \left(\frac{R_1 + R_0}{R_1} \right)$$

$$v_e + \frac{R_0 v_e}{R_1} - v_s = 0 \Rightarrow v_s = \left(1 + \frac{R_0}{R_1} \right) v_e$$

$$v_{smax} = \left(1 + \frac{R_0}{R_1} \right) v_{Emax} = 50 \times 200 \cdot 10^{-3} = 10 \text{ V}$$

$$i_{bmax} = 30 \text{ mA} \Rightarrow i_{Emax} = (\beta + 1) i_{bmax} \approx 3 \text{ A}$$

$$i_{smax} = i_{Emax} - \frac{v_{Emax}}{R_1} = 3 - \frac{200 \cdot 10^{-3}}{1 \cdot 10^4} = 3 - 20 \cdot 10^{-6} \approx 3 \text{ A}$$

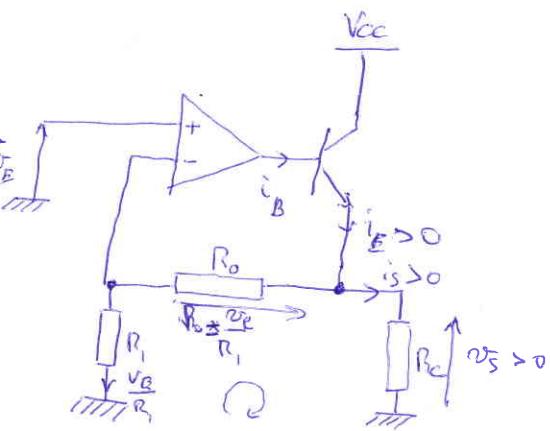

PARTIE 2: 1)


$$u = V^- - v_s = -v_s \Rightarrow i = -C \frac{dv_s}{dt}$$

$$v_e = R_i = RC \frac{dv_s}{dt} \Rightarrow v_s = \frac{1}{RC} \int v_e dt$$

$$V^- = V^+ = 0$$


$$\dot{i} \parallel u \quad i = C \frac{du}{dt}$$

$$V = \frac{\frac{V_E}{R} + v_s j \omega C}{\frac{1}{R} + j \omega C} = 0 \quad \begin{cases} \frac{V_s}{V} = \frac{-V_E}{R + j \omega C} \\ \frac{1}{V_s} = \frac{-R j \omega C}{V_E} \\ \frac{V_E}{V_s} = R j \omega C \end{cases} \quad \begin{cases} \frac{V_s}{V_E} = \frac{-1}{R j \omega C} \\ A(\omega) = |T| = \frac{1}{R j \omega C} \xrightarrow{\omega \gg 0} 0 \\ \Rightarrow \text{Filtre passe-bas} \end{cases}$$

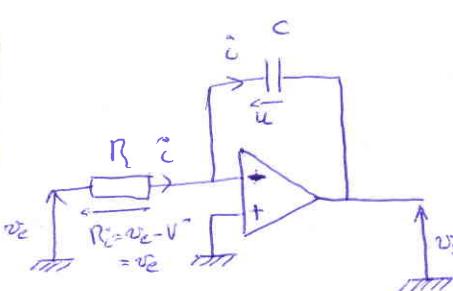


$$V^- = \frac{\frac{V_E}{j \omega C} + \frac{V_s}{R}}{\frac{1}{j \omega C} + \frac{1}{R}} = 0 \Leftrightarrow \frac{V_E}{j \omega C} + \frac{V_s}{R} = 0.$$
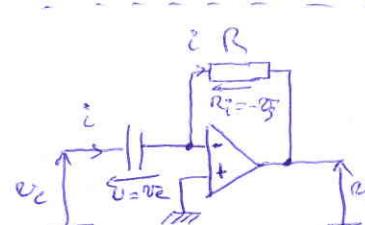
$$\Rightarrow \frac{V_s}{V_E} = -\frac{1}{j \omega C} \times R = -V_E R j \omega C \Leftrightarrow \frac{V_s}{V_E} = -R j \omega C$$



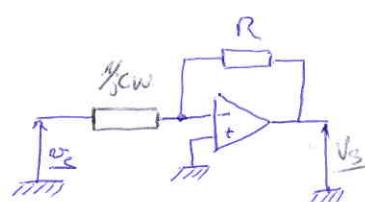
$A(\omega) = R j \omega C \xrightarrow{\omega \gg 0} 0$ \Rightarrow Filtre passe-bas.



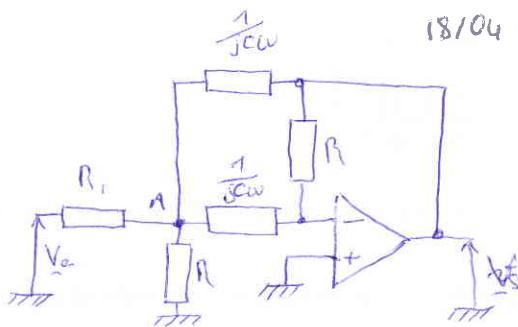4) Miller sur l'entrée.

18/04 ①

$$V_{\text{out}} = \frac{\frac{V_A}{1/jCw} + \frac{V_s}{R}}{\frac{1}{1/jCw} + \frac{1}{R}} = 0.$$



$$jCwV_A + \frac{V_s}{R} = 0$$

$$jR_{\text{CW}}V_A + V_s = 0 \quad (1)$$

Hillman sur A :

$$V_A = \frac{V_e}{R_1} + jCwV_s$$

$$V_A = \frac{1}{R_1 + jCw + jCw + \frac{1}{R}}$$

$$V_A = \frac{RV_e + jR_1R_{\text{CW}}V_s}{R_1 + R_1 + 2jR_1R_{\text{CW}}} \quad (2)$$

(2) \Rightarrow (1)

$$jR_{\text{CW}} \cdot \frac{RV_e + jR_1R_{\text{CW}}V_s}{R_1 + R_1 + 2jR_1R_{\text{CW}}} + V_s = 0$$

$$j^2R_1R_{\text{CW}}^2\omega^2V_s + (R_1 + R_1 + 2jR_1R_{\text{CW}})V_s = -jR_1^2CwV_e$$

$$V_s(R_1 + R_1 + 2jR_1R_{\text{CW}} - R_1R_{\text{CW}}^2\omega^2) = -jR_1^2CwV_e$$

$$T(\omega) = \frac{-jR_1^2Cw}{R_1 + R_1 + 2jR_1R_{\text{CW}} - R_1R_{\text{CW}}^2\omega^2}$$

$$T(\omega) = A_o \cdot \frac{\text{Num}(\omega)}{1 + 2j\sigma \frac{\omega}{\omega_0} - \left(\frac{\omega}{\omega_0}\right)^2}$$

V_D bloquée si $V_D < 0$

si $V_s - V_{\text{out}} < 0$

Exercice n°4


$$\text{cas 1: } V_{\text{out}} = -V_{\text{SAT}}$$

$$V_s + V_{\text{SAT}} < 0$$

$$V_e < -V_{\text{SAT}}$$

\Rightarrow IMPOSSIBLE
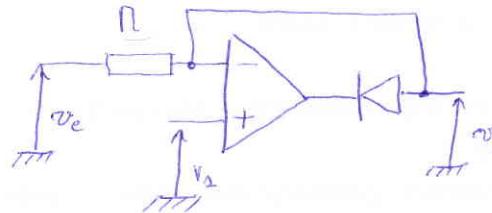
$$\left. \begin{array}{l} \text{or} \\ \left\{ \begin{array}{l} -V_e \leq V_e \leq V_e \\ V_e < V_{\text{SAT}} \end{array} \right. \end{array} \right\} \Rightarrow -V_{\text{SAT}} < V_e < V_{\text{SAT}}$$



$$\text{cas 2: } V_{\text{out}} = V_{\text{SAT}}, \quad \varepsilon > 0$$

$$V_e - V_{\text{SAT}} < 0$$

$V_e < V_{\text{SAT}} \Rightarrow$ OK Possibile

$$\varepsilon > 0 \text{ si } V^+ - V^- > 0 \text{ si } V^+ > V^-$$

$$\text{si } V_i > V_c$$

